



# **LED Drivers**

***A Practical Understanding  
for Lighting Applications***

**Dr. Adan Hernandez, Philips-Advance**


**Al Marble, Philips-Advance**

# Outline

- # **What is a driver?**
- # **Design types**
- # **Constant current vs. constant voltage**
- # **Standards/compliance to codes**
- # **Environmental/temperature ratings**
- # **Power factor correction**
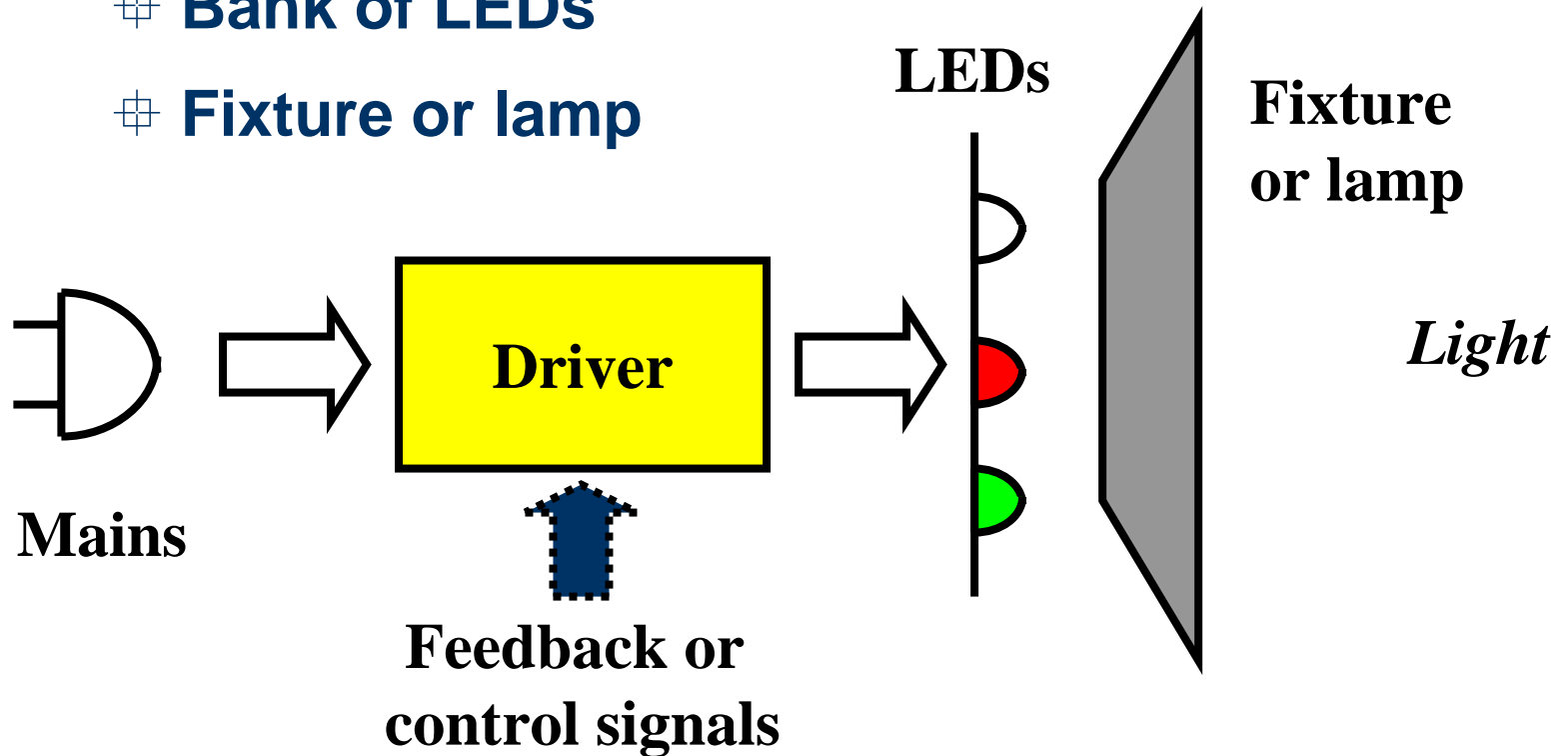
# Typical SSL system

- # Driver
- # Bank of LEDs
- # Fixture or lamp




# Purpose and Function

- ⊠ “Driver” term adopted from electronic component terminology
- ⊠ Similar function as ballast
  - ⊠ Processes line voltage into power usable by LED’s
  - ⊠ Regulates and controls current to LED’s



Switch-mode electronic solutions

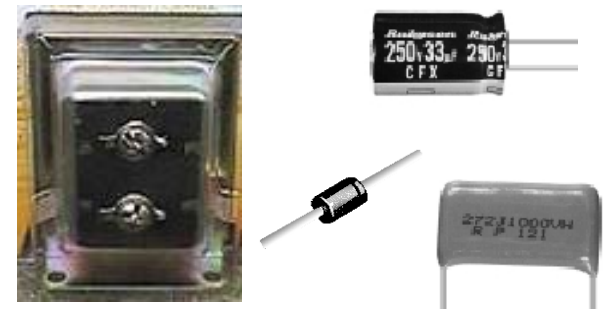

Magnetic solutions

# Resistor/Cap/Diode combination

## ✦ *Example*

- ✦ Film capacitor to drop mains voltage
- ✦ Rectify signal with diodes
- ✦ Use resistor to limit current

## ✦ *Advantages*

- ✦ Inexpensive & small

## ✦ *Disadvantages*

- ✦ Limited power range
- ✦ Inefficient (~50%)
- ✦ No LED brightness regulation
- ✦ No power factor correction
- ✦ Susceptible to line transients
- ✦ High LED ripple current (high crest factor)



# Design Type: Magnetic

## ⊕ Example

- ⊕ Use 60Hz step down transformer
- ⊕ Rectify signal with diode bridge
- ⊕ Use capacitor to filter ripple

## ⊕ Advantages

- ⊕ Low cost (?)

## ⊕ Disadvantages

- ⊕ Limited LED current regulation
- ⊕ Weight & Size
- ⊕ Low power factor
- ⊕ Power de-rating
- ⊕ Safety concerns



# Design Type: Switch-Mode Electronic

## ⊞ Example

- ⊞ Flyback converter
- ⊞ PF correction IC
- ⊞ MOSFET or BJT switch

## ⊞ Advantages

- ⊞ High efficiency
- ⊞ Small size & weight
- ⊞ Power factor correction
- ⊞ Regulation & Controllability


## ⊞ Disadvantages

- ⊞ Higher cost (?)


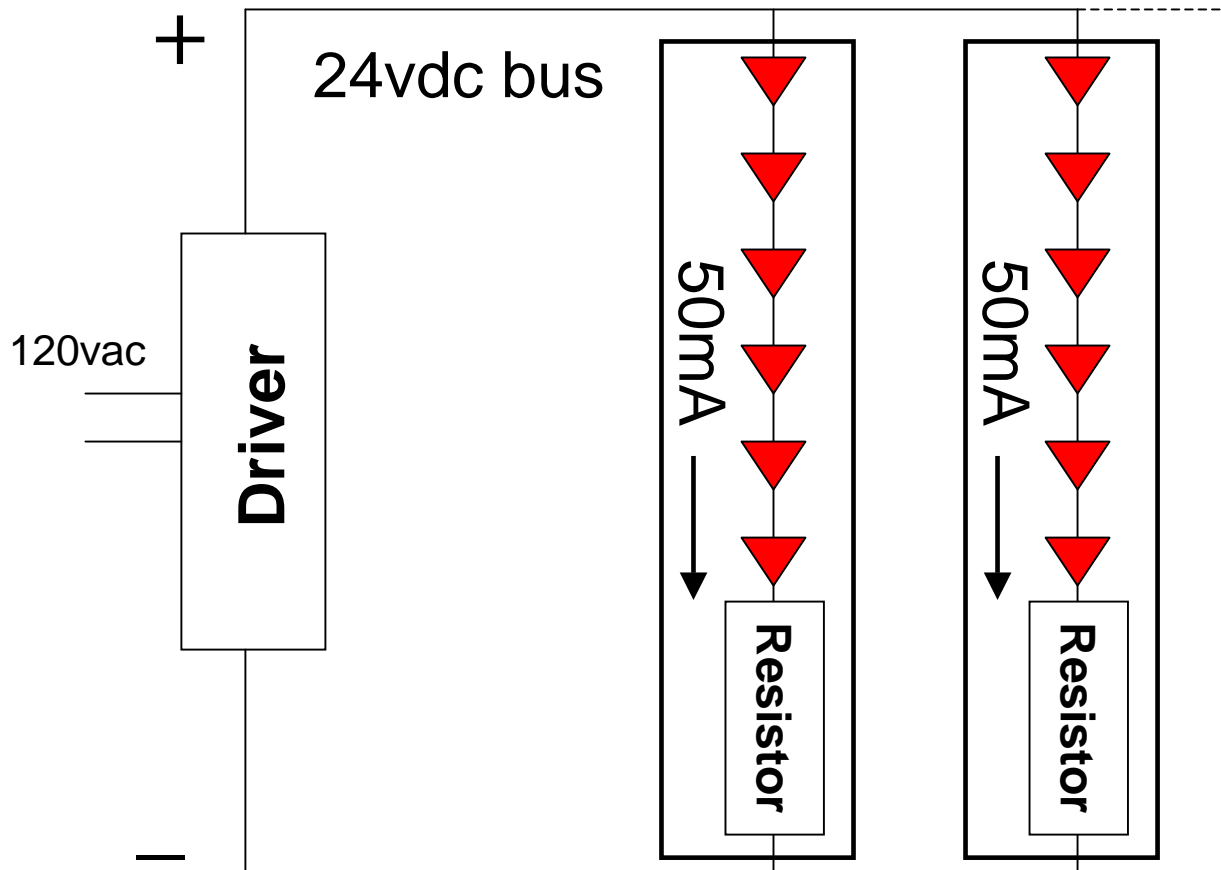
# Operation Type: Voltage Regulated

- # Fixed output voltage (12vdc or 24vdc)
- # Load up to max current/power rating





# Operation Type: Voltage Regulated

## ⊠ Advantage


- ⊠ Flexibility to connect variable LED load
- ⊠ Simple application

## ⊠ Disadvantage

- ⊠ More parts on LED array (current limiting resistors)
- ⊠ Not as energy efficient
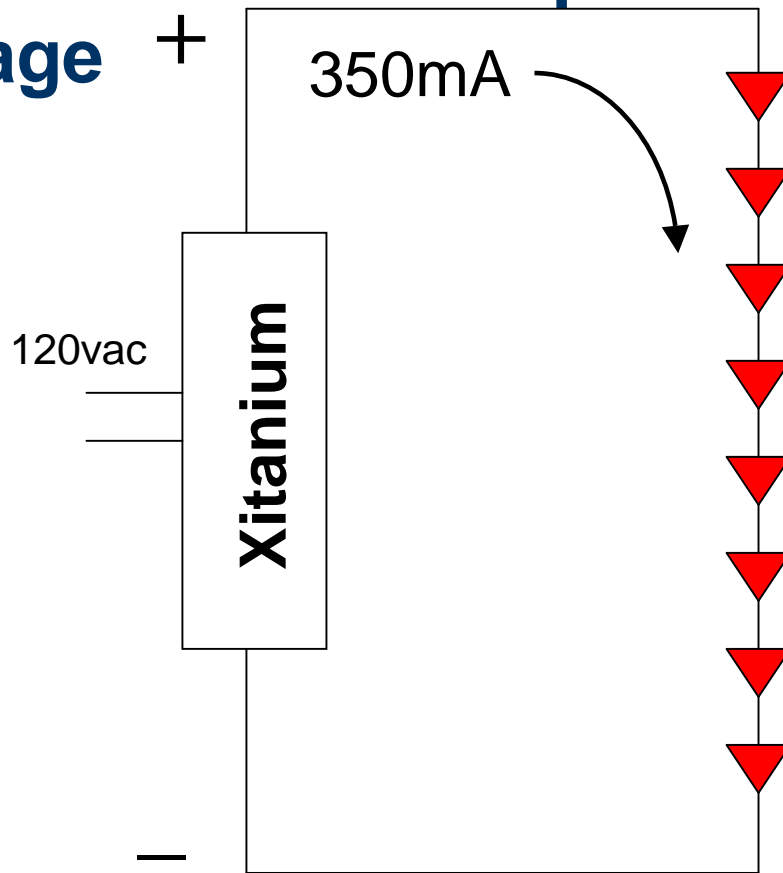
# Operation Type: Current Regulated

- ⊕ **Fixed output current (e.g., 350mA)**
- ⊕ **Add load in series up to max output voltage**



# Operation Type: Current Regulated

## ⊠ Advantage

- ⊠ Greater energy efficiency (no current limiting resistors)

## ⊠ Disadvantage

- ⊠ Less flexibility in connecting variable number of LEDs

## ⊠ In general,

- ⊠ Constant Current for high flux LEDs and,
- ⊠ Constant Voltage for low flux LEDs

# Standards/Compliance to Codes



## ⊕ **UL “Recognized Component” status**

- ⊕ UL not providing “Listing” for LED drivers
- ⊕ Key: Listing in Sign Accessory Manual (SAM)
- ⊕ Confusing to field inspectors

## ⊕ **UL Class 2 (defined in UL 1310)**

- ⊕ Load voltage <30vdc, load current <5 amps
- ⊕ Short circuit protection: Secondary fusing or inherent power limitation
- ⊕ Implies conduit on secondary not required, but many local codes require anyways

# Environmental/Temperature Ratings

## ⊠ Environmental ratings

- ⊠ Dry location: Protected from any moisture
- ⊠ Damp location: Suitable for self-contained signs/raceway installation
  - ※ Mount ½-inch from bottom of enclosure!
  - ※ Referred in UL 935 as “Outdoor Type II”
- ⊠ Wet location: Weatherproof housing/enclosure

## ⊠ Temperature ratings

- ⊠ Case ratings used by OEMs, impractical for field use
- ⊠ Look for ambient rating for sign application

# Power Factor Correction

- ⊕ **Best understood by thinking of it as “current factor correction”**
  - ⊕ Power factor corrected drivers have lower input amperage draw
  
- ⊕ **Lighting industry standards**
  - ⊕ High power factor (HPF): >90%
  - ⊕ Normal power factor (NPF): <90...60% typical

# Power Factor Correction

## Concept:

For a given LED load . . . HPF driver draws less input amps than NPF driver

⊕ Power factor correction is not related to:

- × Wattage
- × Power supply losses (efficiency)
- × How the LEDs are driven

# Power Factor Correction

## 60 Watt HPF Driver

From Utility:

75 watt **0.7 amp** 120vac



LED Load:

60 watt 5 amp 12vdc



## ⊕ 60 Watt NPF Driver

From Utility:

75 watt **1.0 amp** 120vac



LED Load:

60 watt 5 amp 12vdc





# Power Factor Correction

## Who cares?

### ⊠ The utility

- ⊠ User pays utility for “wattage” (i.e., input power)
- ⊠ Utility must generate “amperage,” so NPF with higher amperage more costly to utility for the same money received from customer



# Power Factor Correction

## Who cares?

# Anyone concerned with the environment

Less amperage



Less generation requirement



Less pollutants

# What to look for in a Driver

## ⊠ Performance

- ⊠ Regulated output
- ⊠ Power factor correction
- ⊠ Efficiency

## ⊠ Size

## ⊠ Life and Reliability

## ⊠ Environmental concerns

- ⊠ Temperature range
- ⊠ Dry, damp, or wet location

## ⊠ Safety

- ⊠ UL Recognition/SAM listing
- ⊠ Class 2



# Questions?

[www.LEDcentral.com](http://www.LEDcentral.com)